

Interfacing and controlling your bends

Colin Raffel
Circuitastrophe 2008

Interfacing

- More than just switches and knobs
- Modulation of bends
- Automated switching
 - Rhythm
 - New sounds
 - Talking between devices (syncing)

What is a bend?

- Change in resistance
 - Variable
 - Fixed resistance
 - Switched resistance (0 ohms)
- Change in capacitance
- Change in inductance
- Change in voltage
- We will be focusing on the first and last.
- “Other”

Resistive \approx Voltage Controlled

- Digital vs analog circuits
 - Analog = variable
 - Digital = switched
- Controlling analog
 - Control voltages
 - Voltage \gg resistance
- Controlling digital
 - Multiplexers
 - Digital sequencing & switching

What is a control voltage?

- Variable voltage
- Changes some parameter
- Traditionally used in synthesizers
- Typical ranges
 - $\pm 15V$ or $\pm 12V \gg \pm 5V$ or $\pm 10V$
 - $+9V \gg +5V$
 - $+5V \gg +5V$ (digital)
 - Arbitrary

Voltage to resistance

- Vactrols
 - Homebrew
 - Vactec/ParkinElmer
- H11F3
- Other methods
 - No resistance (just CV)
 - Fast switching
 - LM13700

Vactrol - Quick & Dirty

- Simply an LED coupled with an LDR
- Cheap, easy to make in a pinch
- Resistance range depends on LDR
- Doesn't work well for 0 - >5k
- Doesn't work well with fast resistance changes
- May require extra circuitry to work like you want it to

H11F3 - Clean & Precise

- LED coupled with OptoFET
- Roughly \$1 each, no DIY option
- Consistent resistance range unit to unit
- Very large range: 100 ohm - 100M
- Can work with pretty much any range
- Very fast
- Sometimes picky in audio circuits
- May require extra circuitry to work like you want it to

CCR not VCR

- LEDs aren't really voltage controlled
- Resistance depends on current
- Current \approx voltage... sometimes
- In many (simple) cases, no problem
- For precision, and in many other cases, we need extra circuitry

Buffers

- Varying voltage \gg buffer \gg voltage source
- No (very little) output resistance
- When do you need them?
- Play it safe
- Remember clipping
- Transistor vs. op amp vs. CMOS

Some CV circuits

- Voltage dividers
- Simple LFOs (555, square waves)
- Complex LFOs (VC, triangle, saw, etc)
- Envelope controls
- Sequencers
- Other

Side note - Expression pedals

- Non-standardization
- Converting one resistance range to another
- Expression pedals: Just voltage dividers
- With buffers, a voltage source
- With VCRs, a varying resistance
- With an H11F3, any range

When a bend is digital...

- Digital is two states: on/off
- Much simpler and easier to deal with
- Many switches & keypads are really digital inputs
- On/off bends (switched) can be digitally controlled
- Sequencers and square waves are inherently digital

Multiplexers

- Automatic switches
- Normally can switch analog or digital signals
- In a digital circuit, logic can be used instead
- Some common types:
 - CD4051
 - CD4052
 - CD4053
 - CD4066/4016
 - Relays
 - Other/”Special Function”

Synced switching

- Squarewaves: Digital on/off
 - 555
 - CMOS-type
- Flip-flops: Divide by two (by two... by two...)
- Sequencers: Clock signal >> stepped outputs
- Microcontrollers: All of this at once
- Not limited to a single device - fanout

Combining analog & digital

- Digital signals can also control vactrols and H11F3
- Square >> triangle (or anything else) is very hard
- Analog multiplexers can take analog inputs >> analog sequencer
- The ultimate circuit